

Third Semester B.E. Degree Examination, May/June 2010

Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Simplify the given Boolean function by using K-map method and express it in SOP form. Realise logic circuit by using NAND gates only.
 $f(A, B, C, D) = \sum (m(7, 9, 10, 11, 12, 13, 14, 15))$ (06 Marks)
- b. Simplify following Boolean function by using K-map method in POS form:
 $f(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 7)$ (06 Marks)
- c. Find prime implicants for the Boolean expression by using Quine McClusky method.
 $f(A, B, C, D) = \sum (1, 3, 6, 7, 8, 9, 10, 12, 14, 15) + d(11, 13)$ (08 Marks)
- 2 a. Define decoder. Draw logic diagram of 3:8 decoder with enable input. (06 Marks)
- b. Implement the given Boolean function by using 8:1 multiplexer.
 $f(A, B, C, D) = \sum (0, 1, 3, 5, 7, 11, 12, 13, 14)$ (06 Marks)
- c. With a neat diagram, explain the decimal to BCD encoder. (08 Marks)
- 3 a. What are the three different models for writing a module body in verilog HDL? Give example for any one model. (06 Marks)
- b. With truth table and a neat logic diagram, explain full adder implementation. (06 Marks)
- c. Explain how IC 7483 can be used as 4 bit adder/subtractor. (08 Marks)
- 4 a. With transfer characteristic, explain how Schmitt trigger converts a random waveform into a rectangular waveform. (06 Marks)
- b. Explain basic S.R flip-flop by using NOR gate. What is the drawback of S-R flip-flop? How J-K flip-flop is obtained from S-R flip-flop? (08 Marks)
- c. Find out characteristic equations of J-K flip-flop and D flip-flop. (06 Marks)

PART – B

- 5 a. Explain any two types of shift register with waveforms. How Johnson counter is obtained from shift register? (10 Marks)
- b. Design Mod-6 synchronous counter by using J-K flip-flop. Give excitation table of J-K flip-flop, state diagram and state transition table. (10 Marks)
- 6 a. Differentiate between Moore and Mealy model of synchronous sequential circuit. (04 Marks)
- b. Reduce the state transition diagram of Mealy model by row elimination method and implication table method. (16 Marks)

State transition diagram.

 


Fig. Q6 (b)

- 7 a. Explain with neat diagram, R-2R ladder type 4 bit D to A converter. Find out analog output if input is 1100 and $V = +5$ volts. For 10 bit DAC if full scale output is 10.24 volts, what is resolution? (10 Marks)
- b. Explain with a neat diagram, successive approximation type DAC. (10 Marks)
- 8 a. With a neat circuit diagram, explain the operation of a two input TTL NAND gate with totem pole output. (08 Marks)
- b. Explain with a neat diagram, CMOS inverter. (06 Marks)
- c. Explain CMOS characteristics. (06 Marks)

WWW.VTUCS.COM

Third Semester B.E. Degree Examination, December 2010

Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

1.
 - a. Draw the logic circuit whose Boolean equation is $Y = \overline{A + B + C}$, use only NAND gates. (04 Marks)
 - b. Find the minimal sum and minimal product using Karnaugh map.
 $f(a, b, c, d) = \sum m(6,7,9,10,13) + d(1,4,5,11)$ (08 Marks)
 - c. Find the prime implicants for the following function using Quine Mccluskey method:
 $f(a, b, c, d) = \sum m(1,2,8,9,10,12,13,14)$ (08 Marks)
2.
 - a. Implement the following function using a 8 : 1 multiplexer :
 $f(a, b, c, d) = \sum m(0,1,5,6,8,10,12,15)$ (05 Marks)
 - b. Describe the working principle of a 3 : 8 decoder. Realize the following Boolean expressions using the 3 : 8 decoder :
 $F_1(A, B, C) = \sum m(1,2,3,4)$ $F_2(A, B, C) = \sum m(3,5,7)$ (06 Marks)
 - c. What is PLA? How does PLA differ from PAL? (05 Marks)
 - d. Write HDL code for a 4 to 1 Mux considering any model. (04 Marks)
3.
 - a. How is 2's complement representation used to perform subtraction? Give an example. (04 Marks)
 - b. Show how two 7483 can be used to add/subtract two 8 bit numbers. Draw a neat diagram and explain its working. (08 Marks)
 - c. Design a 2 bit fast adder. Give its implementation using gates. (08 Marks)
4.
 - a. Calculate the clock cycle time for a system that uses a clock, that has a frequency of :
 i) 10 MHz ii) 6 MHz iii) 750 KHz (03 Marks)
 - b. With a neat block diagram, explain the working of a Master-Slave JK flip flop. Also write its truth table. (07 Marks)
 - c. Explain the function of the circuit shown here with the state transition diagram. (10 Marks)

 


Fig. Q4(c)

PART – B

- 5 a. Draw the logic diagram of a 4 bit serial in serial out shift register using JK flip flop and explain its working with an example. (05 Marks)
 b. Give the HDL code for a shift register of 5 bits constructed using D flip flops. (03 Marks)
 c. Construct a mod 8 asynchronous counter and write the truth table and draw waveforms. (06 Marks)
 d. Design a mod 4 synchronous counter using a –ve edge triggered JK flip flop. Draw the state transition diagram. (06 Marks)

- 6 a. For the following state transition diagram, design equations for Moore model and generate the circuit diagram. (10 Marks)

 


Fig.Q6(a)

- b. Design an asynchronous sequential logic circuit for state transition diagram shown below:

 


Fig.Q6(b)

- c. How does state transition diagram of a Moore machine differ from Mealy machine? (06 Marks)
 (04 Marks)
- 7 a. Draw a binary ladder network for a digital input 1000 and obtain its equivalent circuit. (06 Marks)
 b. Explain the concept of “successive approximation” of a A/D converter. (08 Marks)
 c. In a 8 bit counter type A/D converter driven by 500 KHz clock, find : (06 Marks)
 i) Conversion time
 ii) Average conversion time
 iii) Maximum conversion time.
- 8 a. Explain the working of CMOS NAND, NOR gates. (08 Marks)
 b. Explain with a neat diagram, working of a 2 input NAND gate TTL with totempole output. (07 Marks)
 c. Explain how transistor acts as a switch. Define power dissipation and propagation delay time. (05 Marks)
