

- 6 a. What are necessary conditions for loop gain and phase shift for sustained oscillations according to Barkhausen criterion? (04 Marks)
- b. Explain the working of an Astable multivibrator using IC 555 timer with circuit diagram and relevant waveforms. (08 Marks)
- c. Explain the working of RC low pass RC high pass circuit. (08 Marks)
- 7 a. Explain the steps involved in custom design of mains transformer. (06 Marks)
- b. What are SMPS? Compare linear power supplies with SMPS. (07 Marks)
- c. Explain the working of three terminal voltage regulators. (07 Marks)
- 8 a. What should be the slew rate chosen for an OPAMP as an inverting amplifier configuration with gain of 10 when input is a sinusoidal signal with peak to peak value of 2V and highest frequency expected is 50 Hz? (04 Marks)
- b. Explain the working of an OPAMP window comparator with circuit diagram. (08 Marks)
- c. Explain the lead and lag type of phase shifter. (08 Marks)
